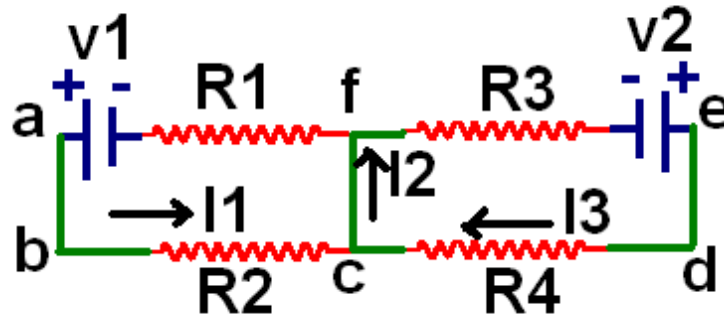


Consider the circuit shown below. Find the currents in each branch.



We have then 2 loops and 1 junction. Kirchoff's laws say:

$$(abcf): v_1 - I_1 R_1 - I_1 R_2 = 0$$

$$(edcfe): v_2 - I_3 R_4 - I_3 R_3 = 0$$

$$@c: I_1 + I_3 - I_2 = 0$$

$$v_1 - I_1 R_1 - I_1 R_2 = 0$$

$$v_2 - I_3 R_4 - I_3 R_3 = 0$$

$$I_1 + I_3 - I_2 = 0$$

Solutions for currents:

$$I_1 = \frac{V_1}{R_1 + R_2}; I_2 = \frac{V_1}{R_1 + R_2} + \frac{V_2}{R_3 + R_4}; I_3 = \frac{V_2}{R_3 + R_4}$$

The answer should not be too much of a surprise.

Note that at Wims, you would enter:

$$V1 - I1 * R1 - I1 * R2 = 0$$


$$V2 - I3 * R4 - I3 * R3 = 0$$

$$I1 + I3 - I2 = 0$$

parameters: R1, R2, R3, R4, V1, V2

Solution:
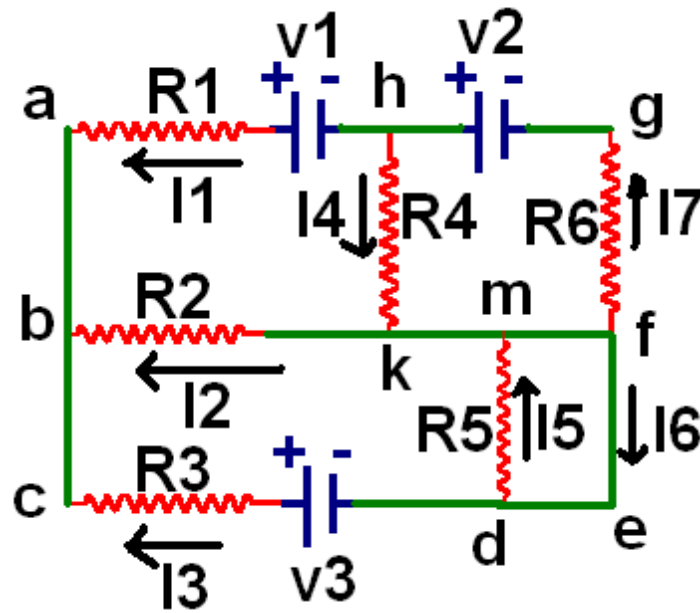
$$\{ i_1 = v_1/(r_2+r_1), i_2 = (r_2 v_2+r_1 v_2+(r_4+r_3) v_1)/(r_2(r_4+r_3)+r_1(r_4+r_3)), i_3 = v_2/(r_4+r_3) \}$$



Needed: 4 loops, 3 junctions
 (abkha): $I_2 R_2 + I_4 R_4 + V_1 - I_1 R_1 = 0$
 (bcdmb): $I_3 R_3 - V_3 - I_5 R_5 - I_2 R_2 = 0$
 (hkfgh): $-I_4 R_4 - I_7 R_6 + V_2 = 0$
 (defmd): $I_5 R_5 = 0$
 @h: $I_7 - I_1 - I_4 = 0$
 @b: $I_1 + I_2 + I_3 = 0$
 @kmf: $I_5 - I_2 - I_6 + I_4 - I_7 = 0$


At Wims, enter:
 $I_2 R_2 + I_4 R_4 + V_1 - I_1 R_1 = 0$
 $I_3 R_3 - V_3 - I_5 R_5 - I_2 R_2 = 0$
 $I_4 R_4 - I_7 R_6 + V_2 = 0$
 $I_5 R_5 = 0$
 $I_7 - I_1 - I_4 = 0$
 $I_1 + I_2 + I_3 = 0$
 $I_5 - I_2 - I_6 + I_4 - I_7 = 0$

With parameters: $R_1, R_2, R_3, R_4, R_5, R_6, V_1, V_2, V_3$


The result is a bit nasty:

$$\{ i_1 = \frac{(-r_2 r_6 v_3 + r_4(r_2(v_2 - v_3) + r_3 v_2) + (r_3 r_6 + r_2 r_6 + (r_3 + r_2) r_4) v_1)}{(r_4(r_2(r_6 + r_3 + r_1) + r_3 r_6 + r_1 r_3) + r_2(r_3 r_6 + r_1 r_6) + r_1 r_3 r_6)}, i_2 = \frac{-(r_4(r_6 v_3 + r_1 v_3 + r_3 v_2) + r_1 r_6 v_3 + (r_3 r_6 + r_3 r_4) v_1)}{(r_4(r_2(r_6 + r_3 + r_1) + r_3 r_6 + r_1 r_3) + r_2(r_3 r_6 + r_1 r_6) + r_1 r_3 r_6)}, i_3 = \frac{-(r_4(-r_6 v_3 - r_1 v_3 + r_2(v_2 - v_3)) - r_2 r_6 v_3 - r_1 r_6 v_3 + (r_2 r_6 + r_2 r_4) v_1)}{(r_4(r_2(r_6 + r_3 + r_1) + r_3 r_6 + r_1 r_3) + r_2(r_3 r_6 + r_1 r_6) + r_1 r_3 r_6)}, i_4 = \frac{-(r_2(-r_6 v_3 - r_3 v_2 - r_1 v_2) - r_1 r_3 v_2 + (r_3 r_6 + r_2 r_6) v_1)}{(r_4(r_2(r_6 + r_3 + r_1) + r_3 r_6 + r_1 r_3) + r_2(r_3 r_6 + r_1 r_6) + r_1 r_3 r_6)}, i_5 = 0, i_6 = \frac{-(r_4(-r_6 v_3 - r_1 v_3 + r_2(v_2 - v_3)) - r_2 r_6 v_3 - r_1 r_6 v_3 + (r_2 r_6 + r_2 r_4) v_1)}{(r_4(r_2(r_6 + r_3 + r_1) + r_3 r_6 + r_1 r_3) + r_2(r_3 r_6 + r_1 r_6) + r_1 r_3 r_6)}, i_7 = \frac{(r_4(r_2(v_2 - v_3) + r_3 v_2) + r_2(r_3 v_2 + r_1 v_2) + r_1 r_3 v_2 + (r_3 + r_2) r_4 v_1)}{(r_4(r_2(r_6 + r_3 + r_1) + r_3 r_6 + r_1 r_3) + r_2(r_3 r_6 + r_1 r_6) + r_1 r_3 r_6)} \}$$

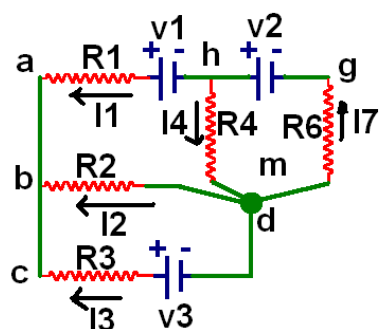You can note that the single solution here for I_5 is zero. This is because the wire (defm) shorts out R_5 . The circuit is therefore can be simplified. In a simpler form, it looks like this:



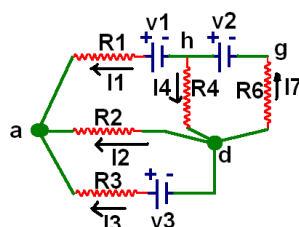We can also simplify the section (abc) so that the circuit looks like this:



Here, we need 3 loops and 2 junctions:

$$(ada): +I_3 \cdot R_3 - V_3 - I_2 \cdot R_2 = 0$$

$$(adha): I_2 \cdot R_2 + I_4 \cdot R_4 + V_1 - I_1 \cdot R_1 = 0$$

$$(hdgh): -I_4 \cdot R_4 - I_7 \cdot R_6 + V_2 = 0$$

$$@a: I_1 + I_2 + I_3 = 0$$

$$@d: I_4 - I_2 - I_7 - I_3 = 0$$

At Wims:

$$I_3 \cdot R_3 - V_3 - I_2 \cdot R_2 = 0$$

$$I_2 \cdot R_2 + I_4 \cdot R_4 + V_1 - I_1 \cdot R_1 = 0$$

$$-I_4 \cdot R_4 - I_7 \cdot R_6 + V_2 = 0$$

$$I_1 + I_2 + I_3 = 0$$

$$I_4 - I_2 - I_7 - I_3 = 0$$

Parameters: $R_1, R_2, R_3, R_4, R_6, V_1, V_2, V_3$

If you solve these, the results are fairly nasty.

$$\{ i_1 = -(r_2(r_6+r_4) v_3 + r_3((-r_6-r_4) v_1 - r_4 v_2) + r_2((-r_6-r_4) v_1 - r_4 v_2)) / (r_3(r_2(r_6+r_4) + r_4(r_6+r_1) + r_1 r_6) + r_2(r_4(r_6+r_1) + r_1 r_6)), i_2 = -((r_4(r_6+r_1) + r_1 r_6) v_3 + r_3(r_4 v_2 + (r_6+r_4) v_1)) / (r_3(r_2(r_6+r_4) + r_4(r_6+r_1) + r_1 r_6) + r_2(r_4(r_6+r_1) + r_1 r_6)), i_3 = ((r_2(r_6+r_4) + r_4(r_6+r_1) + r_1 r_6) v_3 + r_2((-r_6-r_4) v_1 - r_4 v_2)) / (r_3(r_2(r_6+r_4) + r_4(r_6+r_1) + r_1 r_6) + r_2(r_4(r_6+r_1) + r_1 r_6)), i_4 = (r_2 r_6 v_3 + r_3(r_2 v_2 + r_1 v_2 - r_6 v_1) + r_2(r_1 v_2 - r_6 v_1)) / (r_3(r_2(r_6+r_4) + r_4(r_6+r_1) + r_1 r_6) + r_2(r_4(r_6+r_1) + r_1 r_6)), i_7 = -(r_2 r_4 v_3 + r_3(-r_4 v_2 - r_2 v_2 - r_1 v_2 - r_4 v_1) + r_2(-r_4 v_2 - r_1 v_2 - r_4 v_1)) / (r_3(r_2(r_6+r_4) + r_4(r_6+r_1) + r_1 r_6) + r_2(r_4(r_6+r_1) + r_1 r_6)) \}$$

What if, however, you now asked a question such as: supposing all resistors are the same, what value of V_1 would cause I_1 to become zero?

At Wims, enter:

$$I_3 * R - V_3 - I_2 * R = 0$$

$$I_2 * R + I_4 * R + V_1 - I_1 * R = 0$$

$$-I_4 * R - I_7 * R + V_2 = 0$$

$$I_1 + I_2 + I_3 = 0$$

$$I_4 - I_2 - I_7 - I_3 = 0$$

Parameters: R, V_1, V_2, V_3

I'll assign a value of R to each of these resistors. The result is this:

$$\{ i_1 = -(v_3 - v_2 - 2v_1)/(4r), i_2 = -(3v_3 + v_2 + 2v_1)/(8r), i_3 = (5v_3 - v_2 - 2v_1)/(8r), i_4 = (v_3 + 3v_2 - 2v_1)/(8r), i_7 = -(v_3 - 5v_2 - 2v_1)/(8r) \}$$

$$\text{Notice that } I_1 = \frac{-(V_3 - V_2 - 2V_1)}{4} R$$

If we want I_1 to be zero, then we solve:

$$V_3 - V_2 - 2V_1 = 0 \Rightarrow V_1 = \frac{V_3 - V_2}{2}$$

Notice for this particular case, we would have $I_3 = -I_2$ as is required. Also note that I_4 and I_7 are also the same. Essentially we have broken the circuit into two branches. You can now find the power dissipated in each element of the circuit and the total power dissipated.

You can also find this out at Wims: Enter:

$$I_3 * R - V_3 - I_2 * R = 0$$

$$I_2 * R + I_4 * R + V_1 - I_1 * R = 0$$

$$-I_4 * R - I_7 * R + V_2 = 0$$

$$I_1 + I_2 + I_3 = 0$$

$$I_4 - I_2 - I_7 - I_3 = 0$$


$$I_1 = 0$$

parameters: R, V_2, V_3

$$\text{Solution: } \{ i_1 = 0, i_2 = -v_3/(2r), i_3 = v_3/(2r), i_4 = v_2/(2r), i_7 = v_2/(2r), v_1 = (v_3 - v_2)/2 \}$$

The Wheatstone Bridge Circuit:

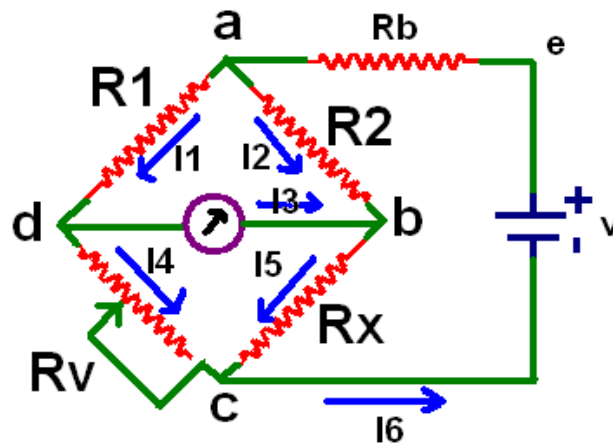Measurement of the unknown resistance R_x .



When the bridge is balanced, I_3 is zero which means there is no potential difference between d and b.

$$(adcea): -I_1 R_1 - I_4 R_v + V - I_6 R_b = 0$$

$$(abcea): -I_2 R_2 - I_5 R_x + V - I_6 R_b = 0$$

$$(adba): -I_1 R_1 - I_3 R + I_2 R_2 = 0$$

$$@a: I_6 - I_1 - I_2 = 0$$

$$@c: I_4 + I_5 - I_6 = 0$$

If at Wims you enter:

$$-I_1 R_1 - I_4 S + V - I_6 B = 0$$

$$-I_2 R_2 - I_5 X + V - I_6 B = 0$$

$$-I_1 R_1 - I_3 R + I_2 R_2 = 0$$

$$I_6 - I_1 - I_2 = 0$$

$$I_4 + I_5 - I_6 = 0$$

Parameters: R, R_1, R_2, V, B, S, X

You will find that the system has infinite solutions. However, if the bridge is balanced, then $I_3 = 0$. So that can be added to the system of equations, but note that if $I_3 = 0$ then $I_1 = I_4$ and $I_2 = I_5$. Add these additional two conditions to the solver gives for I_3 :


$$i_3 = v(r_2 s - r_1 x) / (s(r x + r_2 + b r) + r_1(r x + r_2 + b r) + b(r x + r_2))$$

Which means now that since I_3 is zero, we must have:

$$\text{The unknown resistance: } R_2 R_v - R_1 R_x = 0 \Rightarrow R_x = \frac{R_2}{R_1} R_v$$


Reduction of circuits

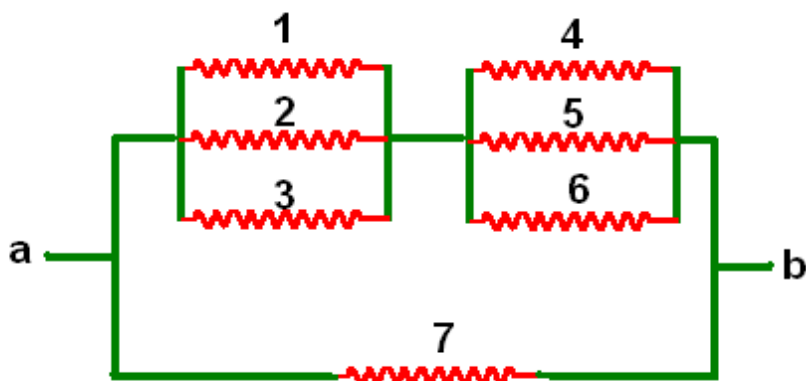It is possible with many simple circuits to reduce the circuits without Kirchoff's laws.
Let me show you some examples of how to do this:




Reduce this circuit in a step-wise method recognizing series and parallel combinations of resistors:

Step 1:

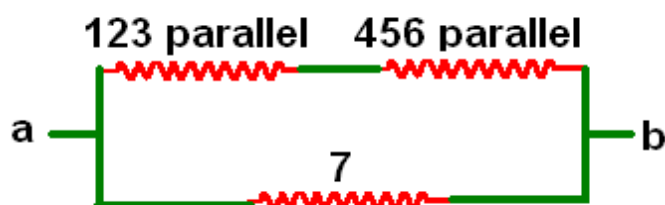

Step2:

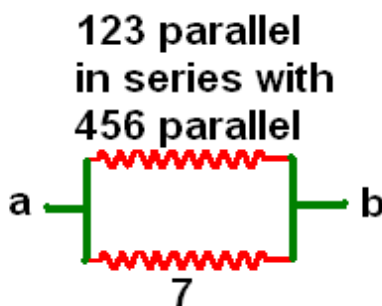

The last step in finding the equivalent resistance is then clear. If you would like to see a numerical example of this, let the resistors be the value of the number that I've assigned to them. Then

$$123 \text{ parallel} = \frac{1}{\frac{1}{1} + \frac{1}{2} + \frac{1}{3}} = \frac{1}{\frac{6}{6} + \frac{3}{6} + \frac{2}{6}} = \frac{1}{\frac{11}{6}} = \frac{6}{11}$$

$$456 \text{ parallel} = \frac{1}{\frac{1}{4} + \frac{1}{5} + \frac{1}{6}} = \frac{1}{\frac{3}{120} + \frac{24}{120} + \frac{20}{120}} = \frac{1}{\frac{74}{120}} = \frac{120}{74}$$


$$(123 \text{ parallel}) \text{ series } (456 \text{ parallel}) = \frac{6}{11} + \frac{120}{74} = \frac{444 + 1320}{814} = \frac{1764}{814}$$

The final step is to calculate the equivalent resistance of the last 2:

$$R_{\text{eq}} = \frac{1}{\frac{1764}{814} + \frac{1}{7}} = \frac{1}{\frac{12348 + 814}{5698}} = \frac{5698}{13162} = 0.43 \Omega$$


You can work backwards from here to find the current through each resistor. It is somewhat important to be able to recognize these series and parallel combinations of resistors.

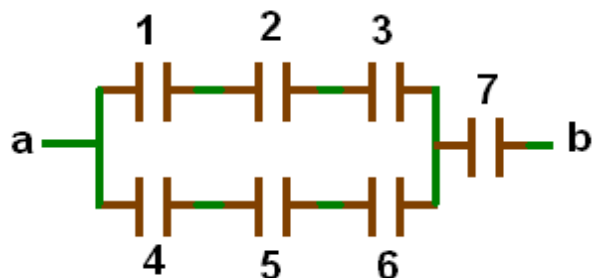The same technique also works for capacitors.
in fact, it the same only different what is the equivalent capacitance of this circuit?




where each of the capacitances is given in μf ? (without doing further calculations)
The answer after you think about it for a while is clearly $0.43 \mu\text{f}$.

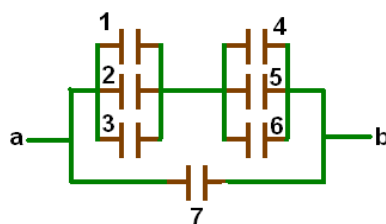Let's do the same thing for a similar arrangement of capacitances:




The first reduction is:

123 parallel 456 parallel

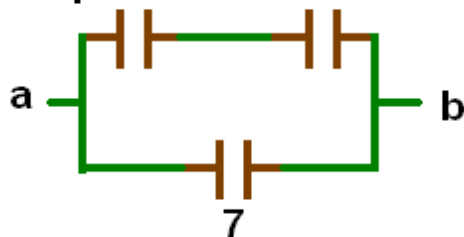

Then

**123 parallel
series
456 parallel**

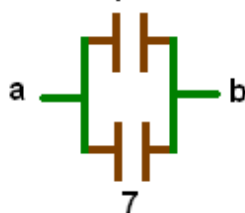

You can calculate this equivalent capacitance:

$$(123 \text{ parallel}) = 1 + 2 + 3 = 6 \mu\text{f}$$


$$(456 \text{ parallel}) = 4 + 5 + 6 = 15 \mu\text{f}$$

$$(123 \text{ parallel}) \text{ series } (456 \text{ parallel}) = \frac{1}{\frac{1}{6} + \frac{1}{15}} = \frac{1}{\frac{15}{90} + \frac{6}{90}} = \frac{90}{21}$$

The equivalent capacitance is then given by:

$$\frac{90}{21} + 7 = 11.29 \mu\text{f}$$

Ok, what about this circuit

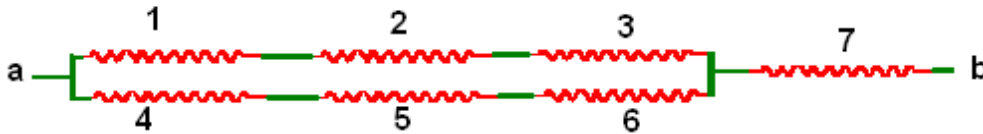

Without calculation, if the numbers represent Ohms, then the equivalent resistance is
11.29Ω

Unfortunately, these types of identifications (i.e. the connection between capacitive and resistive circuits in the analysis) is of limited utility which is why they're probably not often shown.