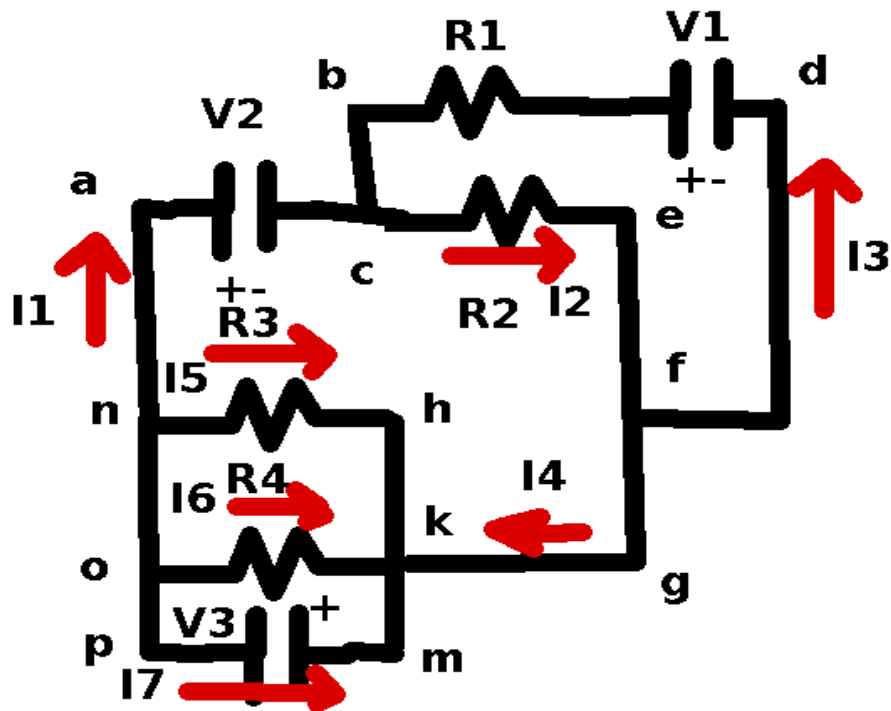


Physics 220: Unquiz 04 r1



Provide the Kirchoff law results for the following:

(bcefdb):

(acefgkhna);

(nhkon):

(okmpo):

@c:

@k:


@f:

If $R_1=1, R_2=2, R_3=3, R_4=4, V_1=10, V_2=20, V_3=30$: the following currents result:

$I_1=-85, I_2=-25, I_3=60, I_4=-85, I_5=-10, I_6=-7.5, I_7=102.5$

Calculate the total power radiated by the circuit.

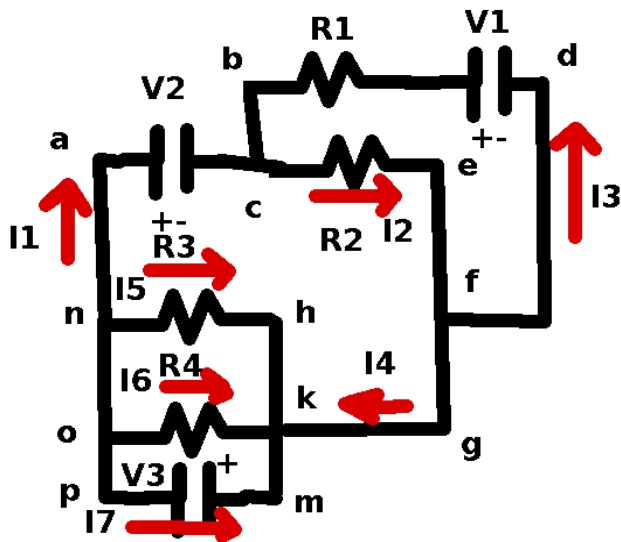What is the interpretation of current I_5 ?



(bcefdb) : $-I_2R_2+V_1-I_3R_1=0$

(acefgkhna): $-V_2-I_2R_2+I_5R_3=0$

(nhkon): $-I_5R_3+I_6R_4=0$

(okmpo): $-I_6R_4 -V_3=0$

@c: $I_1-I_2+I_3=0$

@k: $I_5+I_6+I_7+I_4=0$

@f: $I_2-I_3-I_4=0$

If $R_1=1, R_2=2, R_3=3, R_4=4, V_1=10, V_2=20, V_3=30$:

At the second linear equation solver link: enter:

$-I_2*2+10-I_3*1=0$

$-20-I_2*2+I_5*3=0$

$-I_5*3+I_6*4=0$

$-I_6*4-30=0$

$I_1-I_2+I_3=0$

$I_5+I_6+I_7+I_4=0$

$I_2-I_3-I_4=0$

Obtain: $I_1=-85, I_2=-25, I_3=60, I_4=-85, I_5=-10, I_6=-7.5, I_7=102.5$

What is the total power radiated by the circuit?

$P=I_3^2R_1+I_2^2R_2+I_5^2R_3+I_6^2R_4=60^2*1+25^2*2+10^2*3+7.5^2*4$

$P=3600+1250+300+225=5375W$

What is the interpretation of current I5?

It is in the direction opposite to that indicated by the arrow of I5 in the diagram.