

## Sample Calculations for lab 04

- (1) Show the addition of series and parallel capacitance. In particular, if a  $20\mu\text{f}$  and a  $30\mu\text{f}$  capacitor are connected in series, calculate (showing steps and units) the series equivalent capacitance.
- (2) Show the addition of series and parallel capacitance. In particular, if a  $20\mu\text{f}$  and a  $30\mu\text{f}$  capacitor are connected in parallel, calculate (showing steps and units) the parallel equivalent capacitance.
- (3) A  $1\text{M}\Omega$  resistor and a  $1\mu\text{f}$  capacitor are connected. If the capacitor is initially at a potential difference of  $10\text{V}$ , determine showing details, with units, the time that it will take until the potential difference drops to  $\frac{1}{2}$  of its original value.